

PROJECT IDEA

Project Title:

Efficient design and analysis of secure CMOS logic through logic encryption.

Group Information:

- 1. Aalolika Roy Chowdhury (190205111)*
- 2. Tonima Rani Ghosh (190205112)*
- 3. Raihan Ahmed (190205114)*
- 4. Md. Idrak Efaz (190205121)*
- 5. Sumaia Akter Ritu (190205123)*

Objective:

The objective of this experiment is to design a CMOS logic through logic encryption which is an efficient method to protect circuits from IP piracy, reverse engineering, and malicious tampering of IC for Trojan insertion. The primary concern in the present-day world is all about hardware trust. The security of computer hardware, in particular, Integrated Circuits (IC), is an important aspect of the overall security of computer systems. The circuit functional behavior has 2 cases and those depends on the value of K (0/1). Here K is the 'key' input which encrypts the circuit. In this project, various types of logical transistor circuits will be designed by the help of Cadence.

Circuit Diagram:

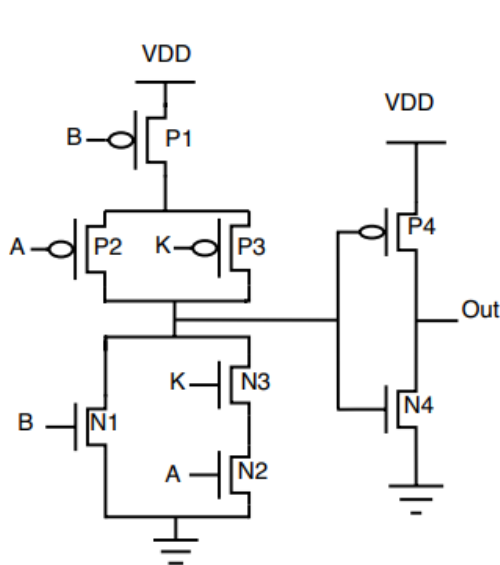


Fig: Secure OR

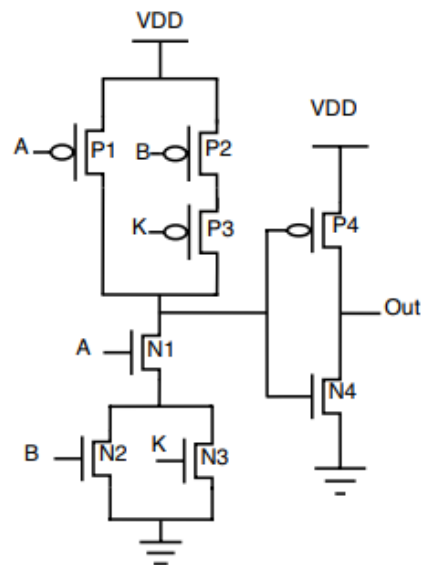


Fig: Secure AND

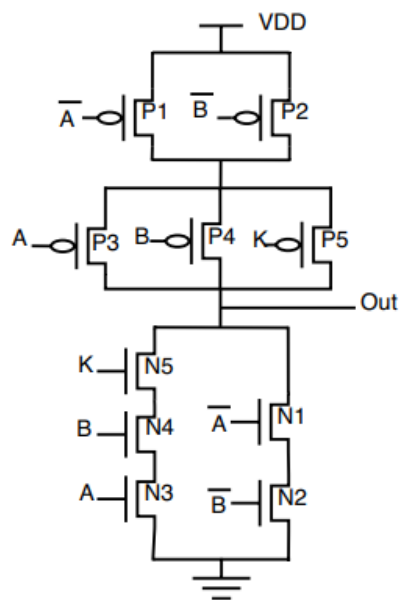


Fig: Secure XOR

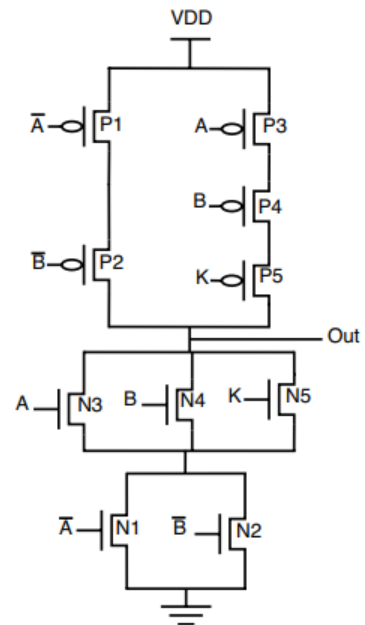


Fig: Secure XNOR

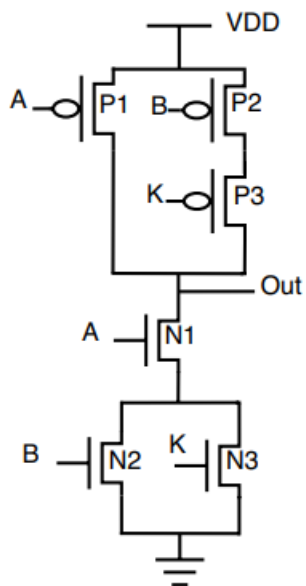


Fig: Secure NAND

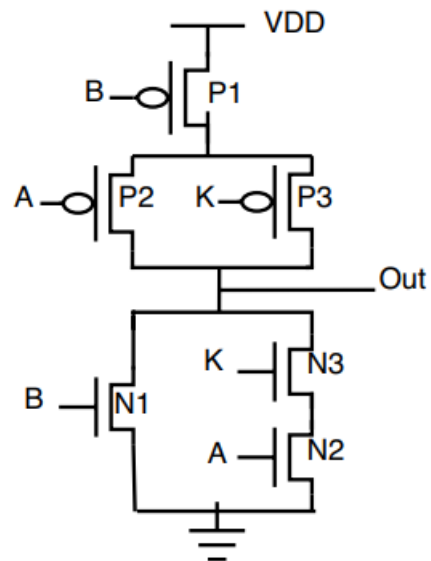


Fig: Secure NOR